
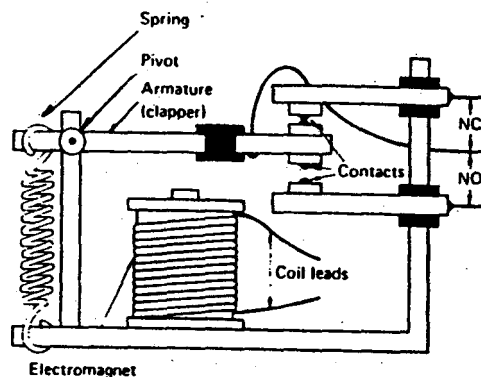


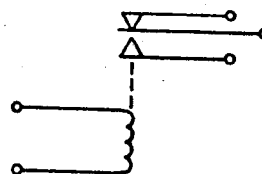

ELECTROMAGNETIC RELAYS





A. Basic Parts of Electromagnetic Relay






B. Schematic Symbol

POWER SYMBOL - SINGLE-POLE DOUBLE-THROW

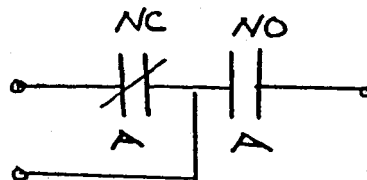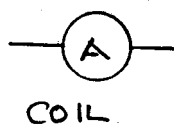

DOUBLE-POLE DOUBLE-THROW

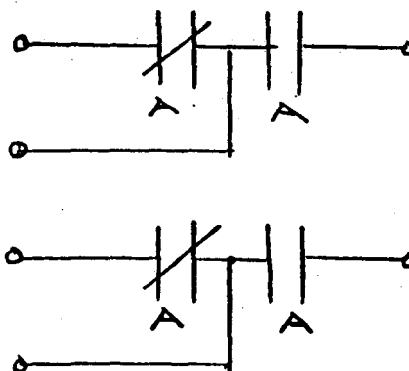
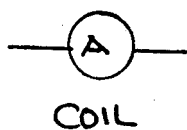


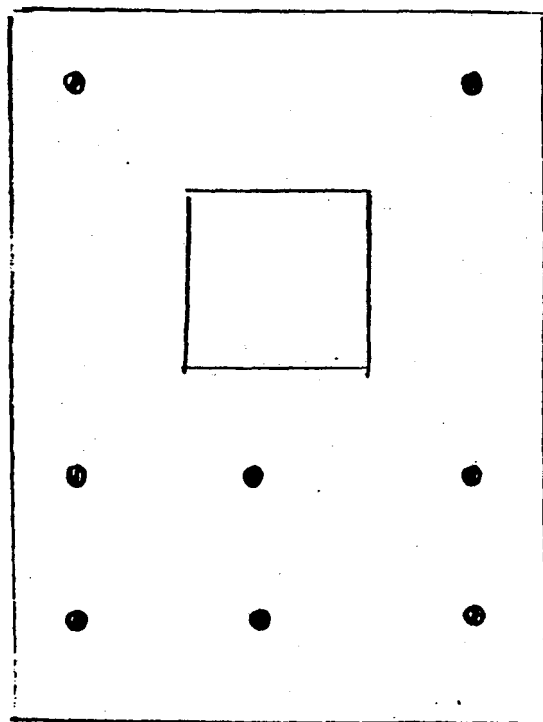


RELAY USED IN EXERCISE ONE.
SKETCH-IN THE COIL & CONTACTS.

RELAY COIL VOLTAGE IS _____.

EXERCISE ONE CIRCUIT #1

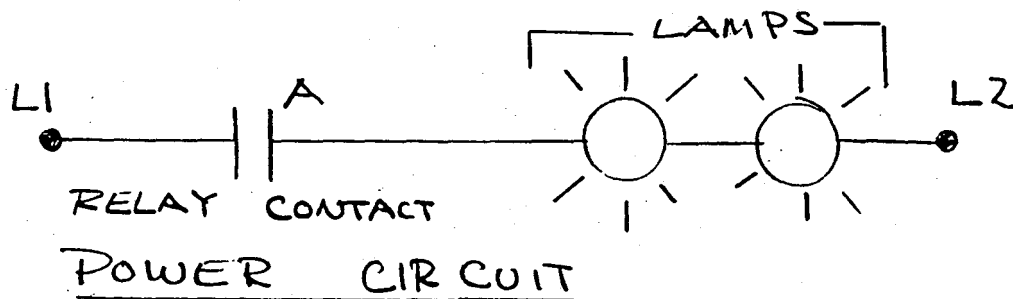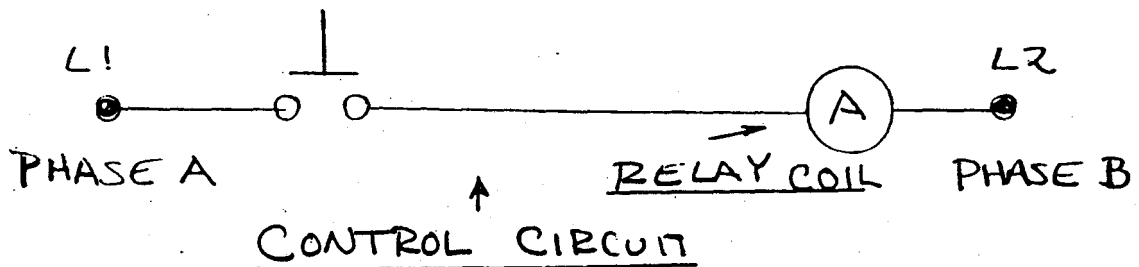

CIRCUIT # 2

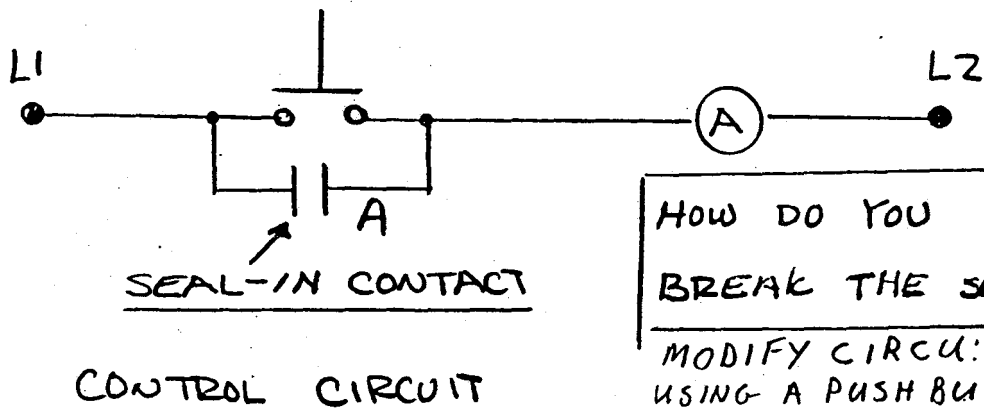

HOW DO YOU
BREAK THE SEAL?

MODIFY CIRCUIT
USING A PUSH BUTTON
TO BREAK THE "SEAL"


NOTE: THE POWER CIRCUIT IS THE SAME AS
THAT GIVEN IN CIRCUIT 1.



* WIRING DIAGRAMS *


"WIRELESS", "LINELESS" OR "TABULAR CONNECTION DIAGRAMS"

EXAMPLE: STANDARD CONTROL CKT.

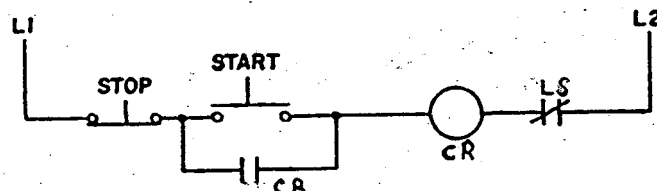


LS = LIMIT SWITCH

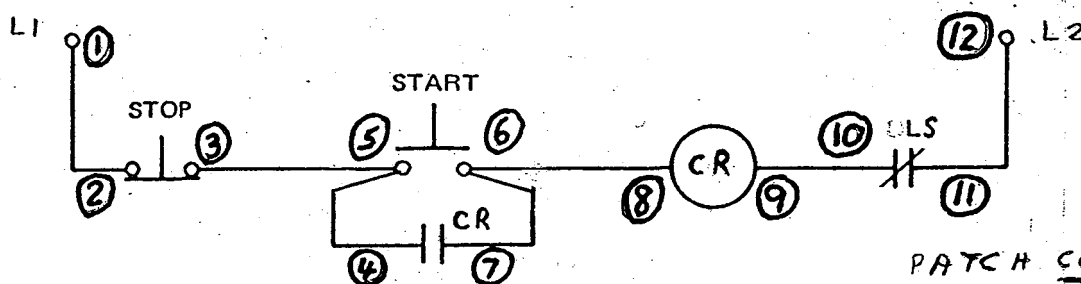REDRAW CKT, LABEL "WIRELESS" CONNECTION ID'S IN ○



PATCH CORD:

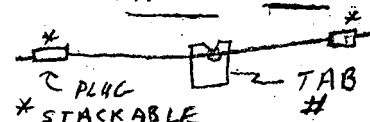


SET UP WIRELESS TABLE

FROM	TO	WIRE ID	TAB #
1	2	RED	—
3	5	BLUE	—
4	5	YEL	—
6	8	RED	1
7	6	RED	2
9	10	BLUE	1
11	12	BLACK	—

USE A UNIQUE TAB # TO DISTINGUISH WIRES OF THE SAME COLOR


SOLID STATE RELAY [SSR]

1. INPUT LADDER DIAGRAM:

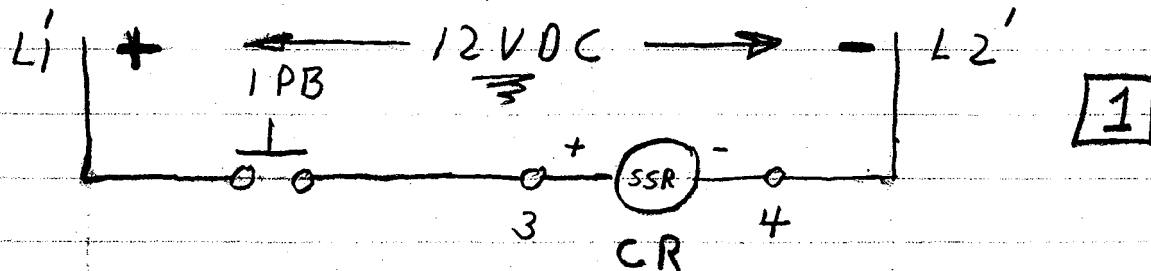

NOTE $\Rightarrow$ TWO DIFFERENT POWER SOURCES ARE USE!

2. OUTPUT LADDER DIAGRAM:

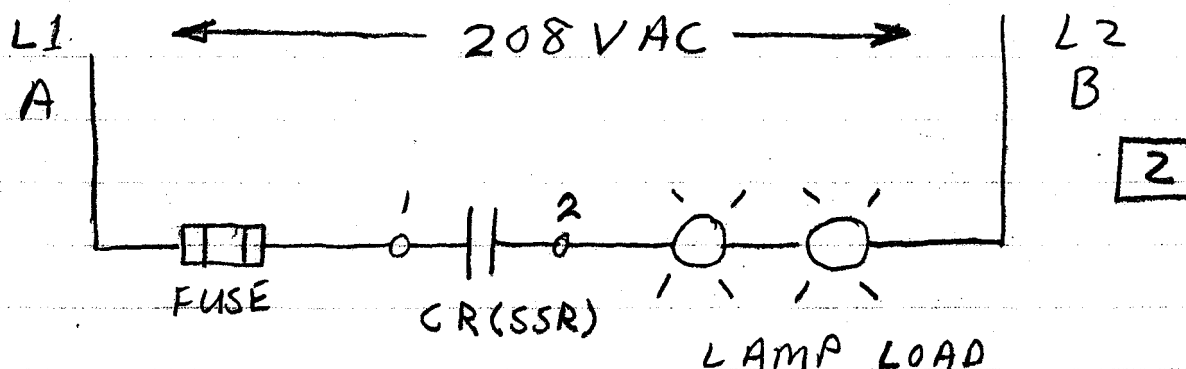

- HAVE EACH GROUP MEMBER CHECK EACH LADDER DIAGRAM. NOTE:
 - #1 LADDER DIAGRAM OPERATES AT 12 VOLTS DIRECT CURRENT (DC).
 - #2 LADDER DIAGRAM OPERATES AT 208 VOLTS ALTERNATING CURRENT (AC).
- UPON INSTRUCTOR APPROVAL; ACTIVATE CRT.

REMOTE CONTROL SYSTEMS (LATCH-UNLATCH COILS)

To control several outlets in a building from each of several different locations, low-voltage operated relays can be installed to turn the 115-volt outlets on or off. The wiring installation for this low-voltage system is less expensive because there is no need to run 115-volt cables to the switches. Low-cost, easily installed #18 or #20 wire is used.

At each controlled outlet, one 24-volt relay is mounted on the outlet box. The relay contains two coils. A momentary current in the *on* coil closes the 115-volt contacts. These contacts remain closed until a momentary current in the *off* coil opens them, Figure 1.

The relay coils are operated from a 24-volt transformer by normally open momentary contact switches. Several of these switches may be connected in parallel to control

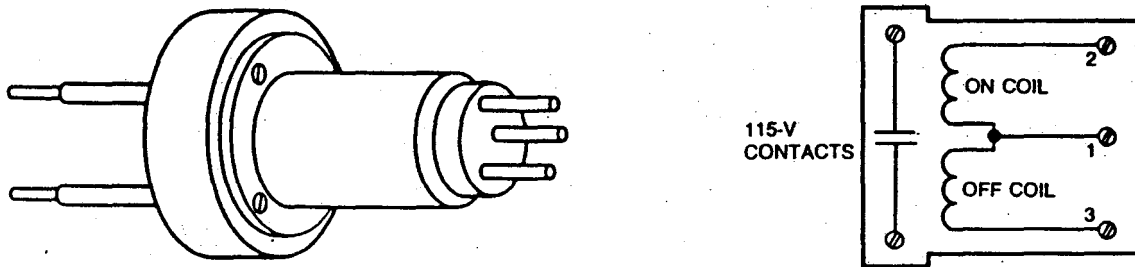


FIGURE 1 Relay connections


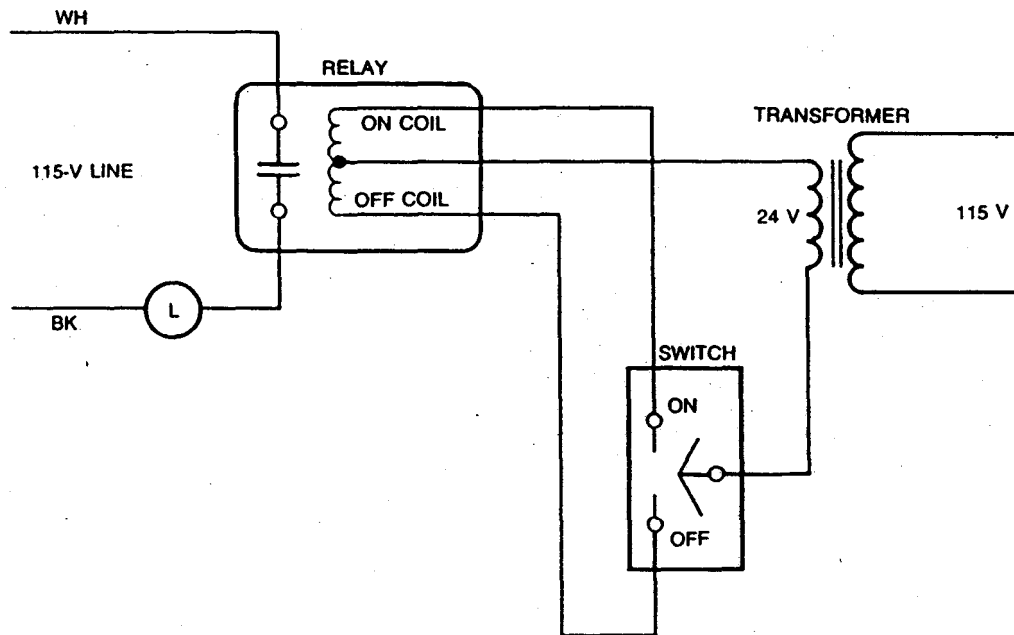


FIGURE 2. One light controlled from one switch point

one relay. The connection of such a switch in the low-voltage circuit is shown in Figure 2.

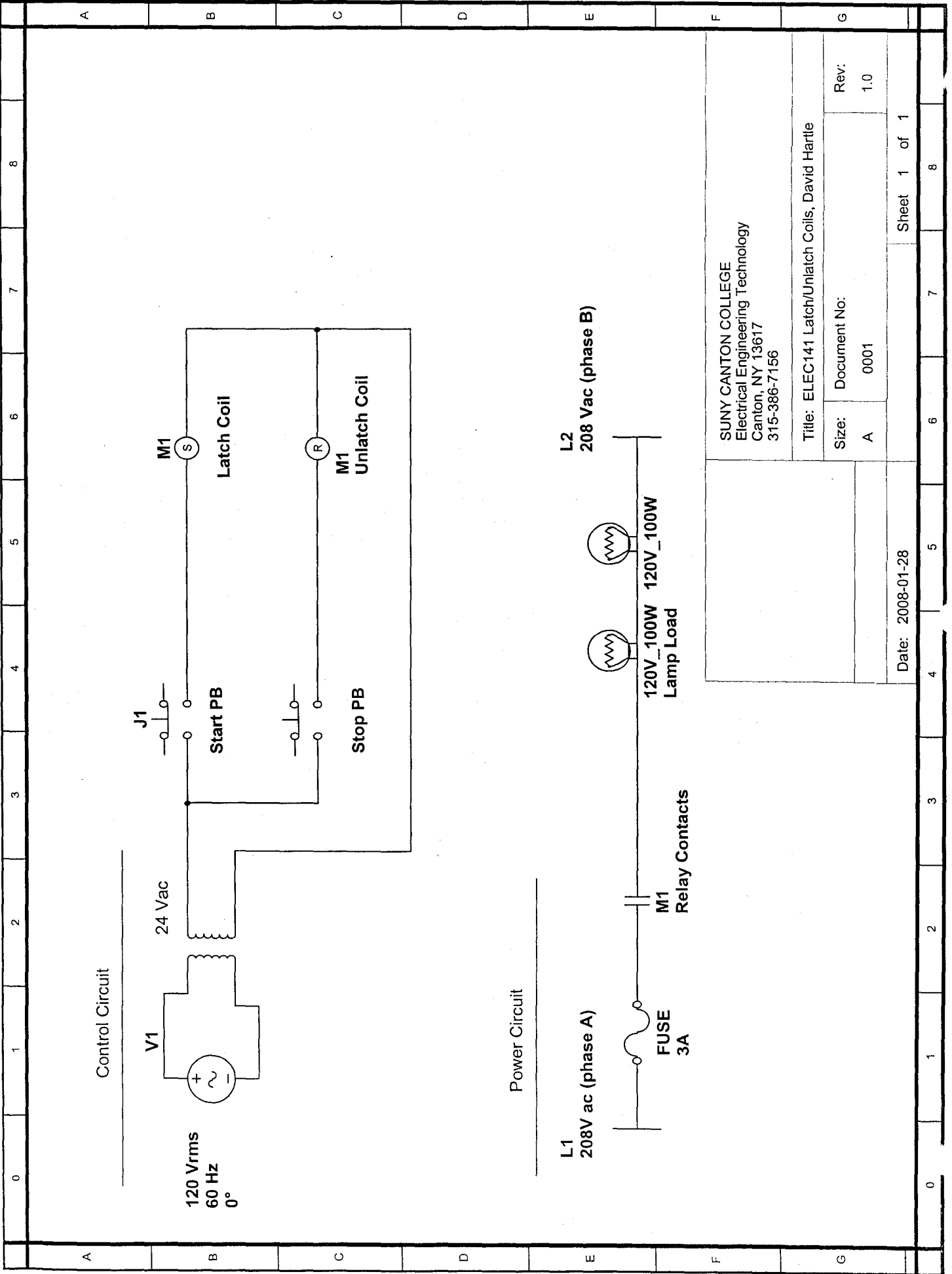Low-voltage systems can be expanded to include a variety of automatic lighting controls, timers, and security systems. In some cases the addition of a rectifier in series with the 24-volt transformer output is recommended. The relay coils then operate on half-wave rectified AC.



SUNY CANTON COLLEGE
Electrical Engineering Technology
Canton, NY 13617
315-386-7156

Title: ELEC141 Latch/Unlatch Coils, David Hartle

Size:	Document No:	Rev:
A	0001	1.0

Date: 2008-01-28

Sheet 1 of 1

