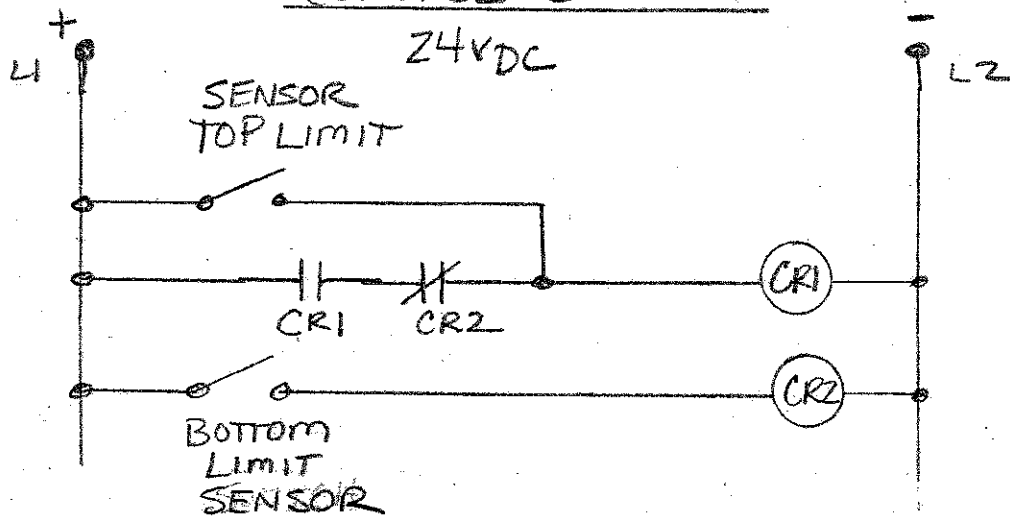



ELEC 141

1 Ø MOTOR CONTROL Z DIRECTION

CONTROL CIRCUIT



POWER CIRCUIT

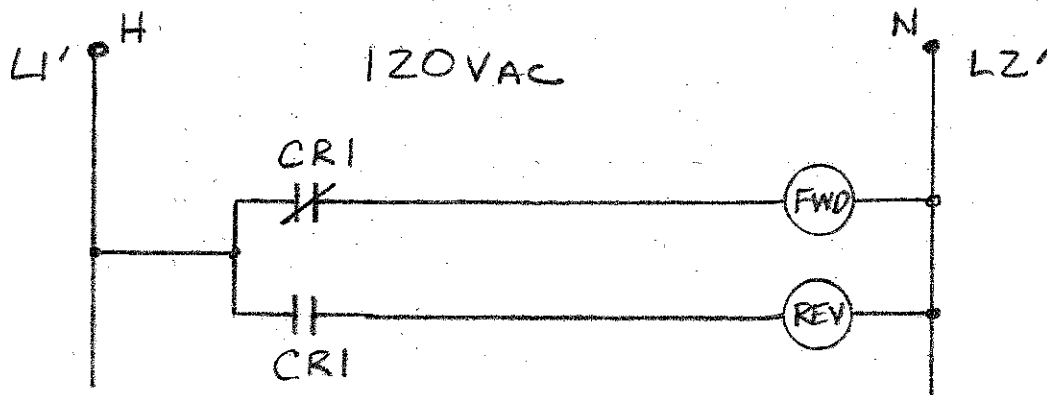

DESIGN PROBLEM 8

ADD 1 STOP + 1 START MOMENTARY PBs AND
CONTROL RELAY TO START/STOP THE
SIMPLE MACHINE